

Final project

Student: Shi Cheng

Student ID: X673894


Course and section: EE 120A Section21

Partner: Yilun Liang



Purpose

The purpose is to make a four-way intersection traffic light using RTL design and Verilog. Some design constraint were that the traffic light only have two light for each way. The constraint is no yellow light and turn signals. The traffic lights is ON for 3 seconds. We need to also add a crosswalk button for pedestrians to cross the road. When you push the crosswalk button, all the traffic light must turn red after three seconds then it allows the pedestrians to cross. The crosswalk is ON for 5 seconds. We used 25MHz to calculate the ticks for the timer.


Circuit Design

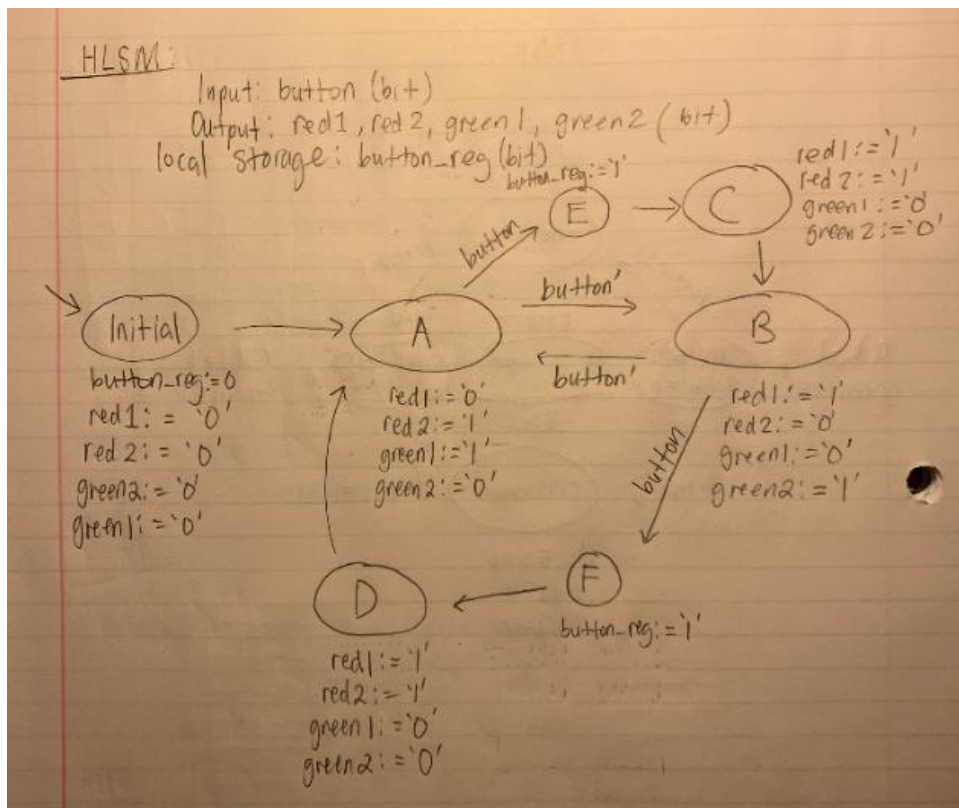

Datapath

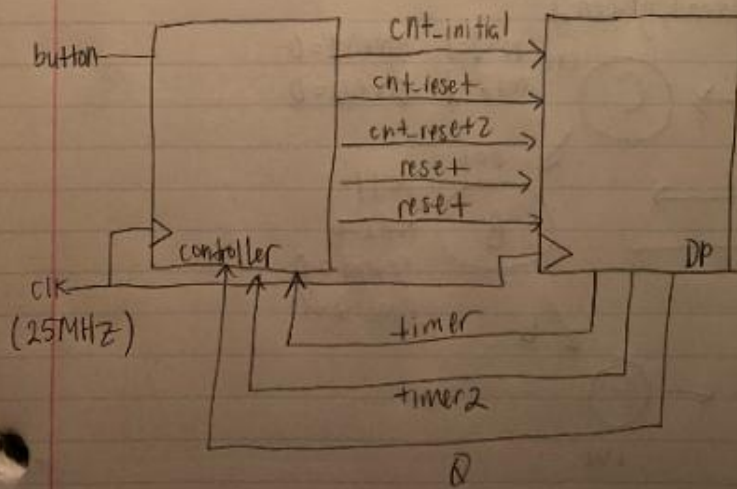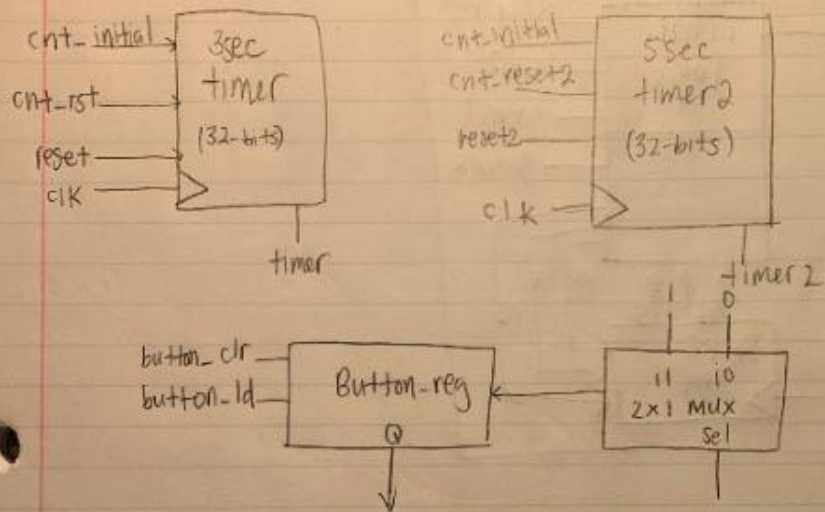


controller

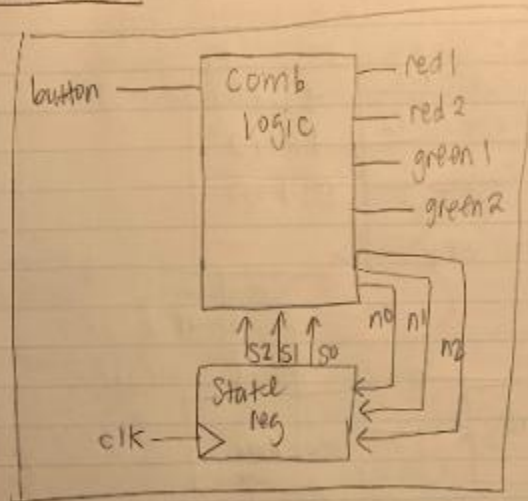

FSM

Input: button

Outputs: red1, red2, green1, green2

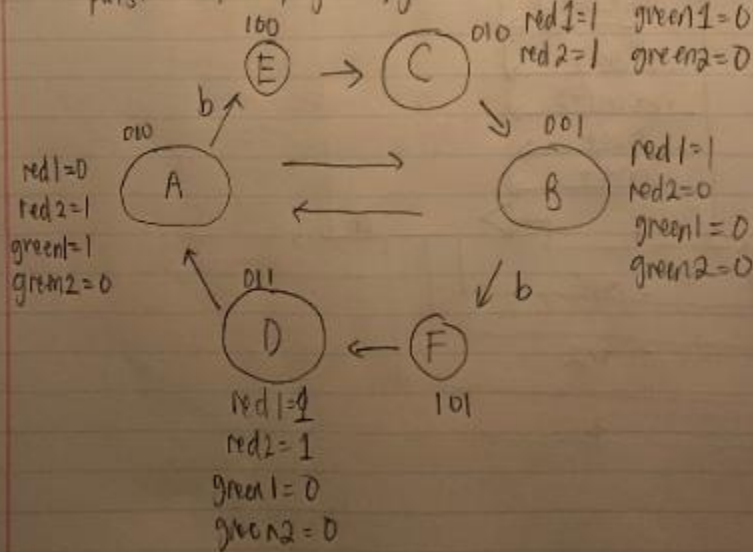

```

module traffic#(
    parameter NBITS=32)
    (
        input clk,
        input button,
        input button2,
        output reg red1,
        output reg red2,
        output reg green1,
        output reg green2
    );

    wire timer;
    wire timer2;
    reg reset=1;
    reg reset2=1;
    wire [NBITS-1:0] cnt_ini;
    wire [NBITS-1:0] cnt_rst1;
    wire [NBITS-1:0] cnt_rst2;
    reg [2:0]current_state= 3'b000;
    reg [2:0]next_state=3'b000;
    reg button_reg = 1'b0;
    reg button2_reg = 1'b0;

    always @(posedge clk) begin
        current_state = next_state;
    end

```

```

assign cnt_ini = 32'h0000;
assign cnt_rst1 = 32'h47868C0;
assign cnt_rst2 = 32'h7735940;

localparam A = 3'b000;
localparam B = 3'b001;
localparam C = 3'b010;
localparam D = 3'b011;
localparam E = 3'b100;
localparam F = 3'b101;
localparam G = 3'b110;
localparam H = 3'b111;

```

```

always @(posedge clk) begin
    case (current_state)
    A: begin
        reset= 0;
        red1 = 0;
        green1 = 1;
        red2 = 1;
        green2 =0;
        if (button == 1)
            begin
                button_reg = 1;
                reset=0;
                next_state = E;
            end
        else if (timer == 1)
            begin

```

```

        reset=1;
        next_state = B;
    end
end
//else
//next_state = A;
//end

B: begin
    reset=0;
    red1 = 1;
    green1 = 0;
    red2 = 0;
    green2 = 1;
    if (button2 == 1)
    begin
        button2_reg = 1;
        reset=0;
        next_state = F;
    end
    else if (timer == 1)
    begin
        reset=1;
        next_state = A;
    end
end

C:begin
    reset2 = 0;
    red1 = 1;
    green1 = 0;
    red2 = 1;
    green2 = 0;
    if (timer2 == 1)
    begin
        reset = 1;
        reset2 = 1;
        next_state = B;
    end
    //else
    //begin
    //next_state=C;
    //end
end

D:begin
    reset2 = 0;
    red1 = 1;
    green1 = 0;
    red2 = 1;
    green2 = 0;
    if (timer2 ==1)
    begin
        reset = 1;
        reset2 = 1;
    end
end

```

```

        next_state = A;
    end
end

E:begin
    reset = 0;
    red1 = 0;
    green1 = 1;
    red2 = 1;
    green2 = 0;
    if (timer == 1 && button_reg == 1)
    begin
        reset = 1;
        reset2 = 1;
        next_state = C;
    end
end

F:begin
    reset = 0;
    red1 = 1;
    green1 = 0;
    red2 = 0;
    green2 = 1;
    if (timer == 1 && button2_reg == 1)
    begin
        reset = 1;
        reset2 = 1;
        next_state = D;
    end
end

G:begin
    reset = 0;
    red1=1;
    green1=0;
    red2 = 0;
    green2=1;
    if (button == 1)
    begin
        button_reg = 1;
        reset=0;
        next_state = E;
    end
end

H: begin
    reset = 0;
    red1 = 0;
    green1 = 1;
    red2 = 1;
    green2 = 0;
    if (button2 == 1)
    begin
        button2_reg = 1;
        reset=0;
        next_state = F;
    end
end

```

```

end

    default: begin
        red1 = 0;
        green1 = 1;
        red2 = 1;
        green2 = 0;
        next_state = B ;
    end

endcase
end

TIMER_ST #( .NBITS(NBITS) ) timerst (
    .timer(timer),
    .clk(clk),
    .reset(reset) ,
    .cnt_ini(cnt_ini),
    .cnt_rst1(cnt_rst1)
);

TIMER_ST #( .NBITS(NBITS) ) timerst2 (
    .timer(timer2),
    .clk(clk),
    .reset(reset2) ,
    .cnt_ini(cnt_ini),
    .cnt_rst1(cnt_rst2)
);|
endmodule

module TIMER_ST #(
    parameter NBITS = 32
)
(
    output wire timer ,
    input wire clk ,
    input wire reset,
    input [NBITS-1:0] cnt_ini ,
    input [NBITS-1:0] cnt_rst1
);
wire [NBITS-1:0] q ;
wire [NBITS-1:0] qnext ;
// Compute the next value
adder #( .NBITS(NBITS) )
    c1 (.q(q),
        .cnt_ini(cnt_ini),
        .cnt_rst1(cnt_rst1),
        .nextq(qnext),
        .tick(timer) );
// Save the next state
floprr1 #( .NBITS(NBITS) )
    c2 (.clk(clk),
        .reset(reset),
        .cnt_ini(cnt_ini),
        .nextq(qnext),
        .q(q) );
endmodule

```



```

module adder#( parameter NBITS = 16 )(
input [NBITS-2:0] q ,
input [NBITS-2:0] cnt_ini ,
input [NBITS-2:0] cnt_rst1 ,
output[NBITS-2:0] nextq,
output tick
);
wire same ;
wire[NBITS-2:0] inextq;
|
addergergen_st #(.NBITS(NBITS))
nextval ( .r(inextq), // Next value
.cout(), // Carry out - Don't use
.a(q), // Current value
.b(16'b0000_0001), // Plus One
.cin(16'b0000_0000) ) ; // No carry in

comparatorgergen_st #(.NBITS(NBITS))
comparator (
.r(same) ,
.a(inextq),
.b(cnt_rst1) );

assign tick = (same) ? 'd1 : 'd0 ;
assign nextq = (same) ? cnt_ini : inextq ;
endmodule

```

```

|module addergergen_st #( parameter NBITS = 16 )(
output wire[NBITS-1:0] r ,
output wire cout ,
input wire[NBITS-1:0] a ,
input wire[NBITS-1:0] b ,
input wire cin ) ;
wire [NBITS:0] carry;
assign carry[0]= cin ;
genvar k ;
generate
for (k=0; k < NBITS; k = k+1)
begin : blk
fulladder_st FA (
.r(r[k]),
.cout(carry[k+1]),
.a(a[k]),
.b(b[k]),
.cin(carry[k]) ) ;
end
endgenerate
assign cout = carry[NBITS] ;
endmodule

```

```

module fulladder_st(
output wire r,
output wire cout,
input wire a,
input wire b,
input wire cin
) ;
assign r = (a ^ b) ^ (cin) ;
assign cout = (a & b) | ( a & cin ) | ( b & cin ) ;
endmodule

```

```

module comparatorgen_st #( parameter NBITS = 16 )(
output wire r ,
input wire[NBITS-1:0] a ,
input wire[NBITS-1:0] b );
wire [NBITS-1:0] iresult ;
genvar k ;
generate
for (k=0; k < NBITS; k = k+1)
begin : blk
xor cl (iresult[k], a[k], b[k] ) ;
end
endgenerate
// Reduction plus negation
assign r = ~(iresult);
endmodule

```

```

module floprl#( parameter NBITS = 16 )(
input clk,
input reset,
input [NBITS-2:0] cnt_ini,
input [NBITS-2:0] nextq,
output[NBITS-2:0] q
);
reg [NBITS-2:0] iq=0 ;
always @(posedge clk) begin
if (reset) begin
iq <= cnt_ini ;
end
else begin
iq <= nextq;
end
end
assign q = iq ;
endmodule

```

UCF:

```

// Inputs
NET "clk" LOC = "B8" ;
NET "button" LOC = "G12" ;
NET "button2" LOC = "M4";
// Outputs
NET "red1" LOC = "G1" ;
NET "green1" LOC = "P4" ;
NET "red2" LOC = "N4" ;
NET "green2" LOC = "N5" ;

```

Testbench:

```
module testbench;

    // Inputs
    reg clk;
    reg button;
    reg button2;


    // Outputs
    wire red1;
    wire red2;
    wire green1;
    wire green2;

    // Instantiate the Unit Under Test (UUT)
    traffic uut (
        .clk(clk),
        .button(button),
        .button2(button2),
        .red1(red1),
        .red2(red2),
        .green1(green1),
        .green2(green2)
    );

    always begin
        #2 clk = ~clk;
    end
    initial begin
        clk = 0;

        // Initialize Inputs
        button = 1;
        #3;

         button2 = 1;
        button = 0;
        #3;
    end
endmodule
```



Problems and Technical Issues

Problems and technical issues encountered were we try to add something where if someone or a pedestrian continues to push the crosswalk button, it will stay in that state. We couldn't get it to work, so we decided to scrap it. Another problem was that we wanted to add the extra button where the traffic lights become red whichever buttons is pressed, but instead we added the extra crosswalk button for their specific traffic light. We had a problem with the waveform from the test bench that looks incorrect because of the timer module.

Conclusion

Our project worked according to our specifications we designed our traffic light system. We were able to design the traffic light using our HLSM design and controller. The HLSM had six states and the data path design had two timer, one for the crosswalk and the traffic light. Some ways to improve the system is to add maybe yellow light and traffic light for the four way and not just two traffic lights. The most difficult part of the project is the coding.

TA problem

How many timers do we use in the project?

Ans: We use two timers. One is for timing 3s, the other one is for timing 5s.